



LOOP COMPENSATION – BUCK CONVERTER DESIGN AND MEASUREMENTS

Robert Schillinger

Field Application Engineer

Mohamed AlAlami

Senior Field Application Engineer

WÜRTH ELEKTRONIK MORE THAN YOU EXPECT

- Control Theory and stability criteria
- Plant Transfer Function
- Compensator Design
- Practical Loop Measurement
 - Bode plots using the oscilloscope
 - Time domain Transient Response



CONTROL THEORY


AND STABILITY

CRITERIA

BASICS OF CONTROL THEORY

Open / Close loop transfer function
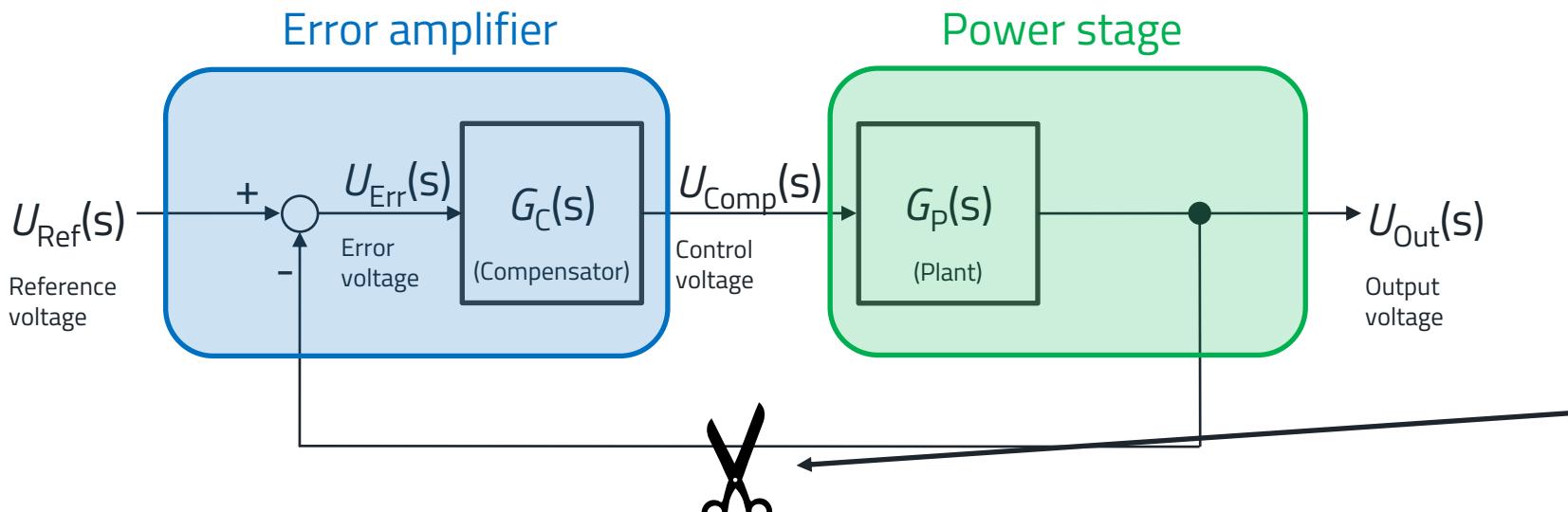
$$\text{transfer function (s)} = \frac{\text{Output (s)}}{\text{Input (s)}}$$



Closed Loop / Block-diagram

- $U_{\text{Ref}}(s)$: Reference voltage = setpoint
- $U_{\text{Err}}(s)$: Error voltage = Error
- $U_{\text{Comp}}(s)$: Control voltage = system input

- $U_{\text{Out}}(s)$: Output voltage = system output

- $G_C(s)$: Transfer function of the compensator
- $G_P(s)$: Transfer function of the plant

- target/actual comparison + compensator = **Error amplifier**

$$G_{\text{OL}}(s) = \frac{U_{\text{Out}}(s)}{U_{\text{Err}}(s)} = G_C(s) \cdot G_P(s)$$

➤ Open loop transfer function


$$G_{\text{CL}}(s) = \frac{U_{\text{Out}}(s)}{U_{\text{Ref}}(s)} = \frac{G_{\text{OL}}(s)}{1+G_{\text{OL}}(s)}$$

➤ Closed loop transfer function

BASICS OF CONTROL THEORY

Identify stability on an open loop bode plot


- **Cross over frequency (bandwidth) - f_x**
 - Frequency at which the gain crosses 0dB („1“)
 - Usually a maximum of 1/10th of the switching frequency is desired
 - **Higher cross over frequency → Faster transient response**
- **Phase margin - φ_M**
 - Phase left to -180° when the gain reaches 0dB
 - Should be $\geq 45^\circ$ (60° preferred)
 - **Lower phase margin → more oscillating in transient response (load step)**
- **Gain margin - G_M**
 - Gain below 0dB when the phase reaches -180° („-“)
 - 10-15dB is considered good
 - **Gain margin too low → low variation robustness → oscillations could be the result**

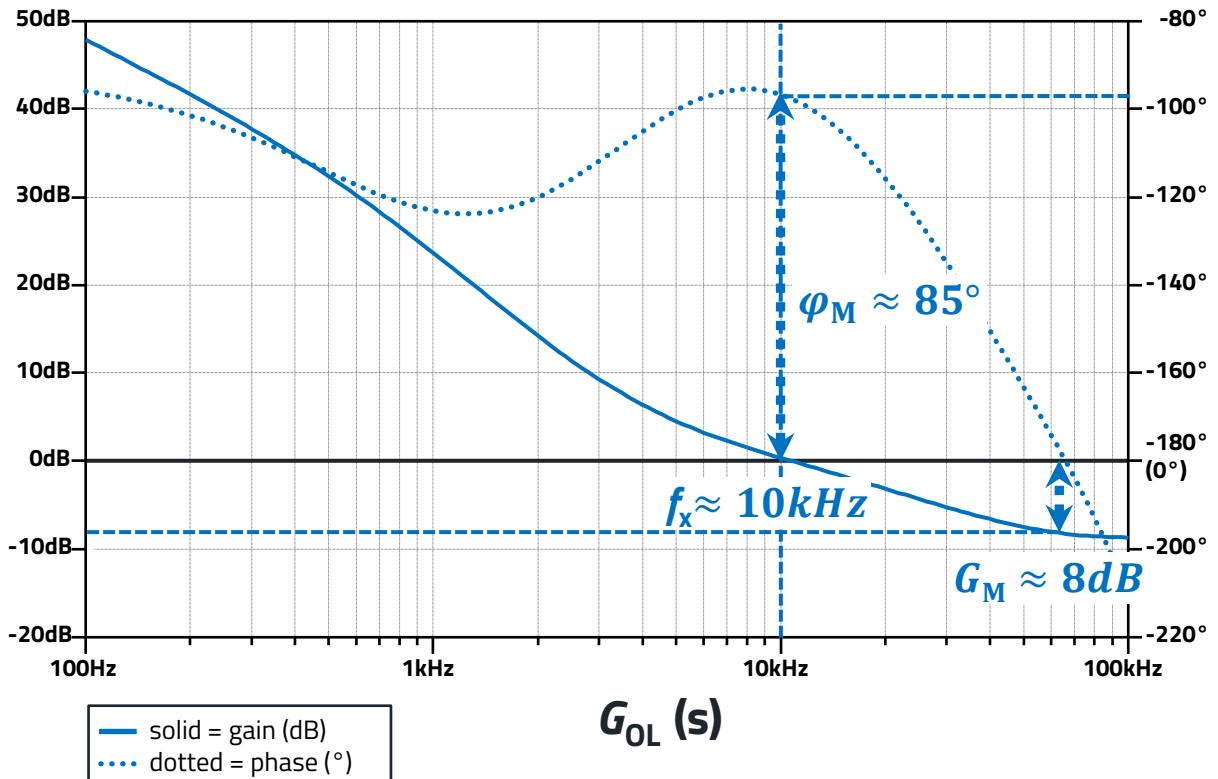


Typical bode plot – Open loop

IMPACT OF PHASE MARGIN

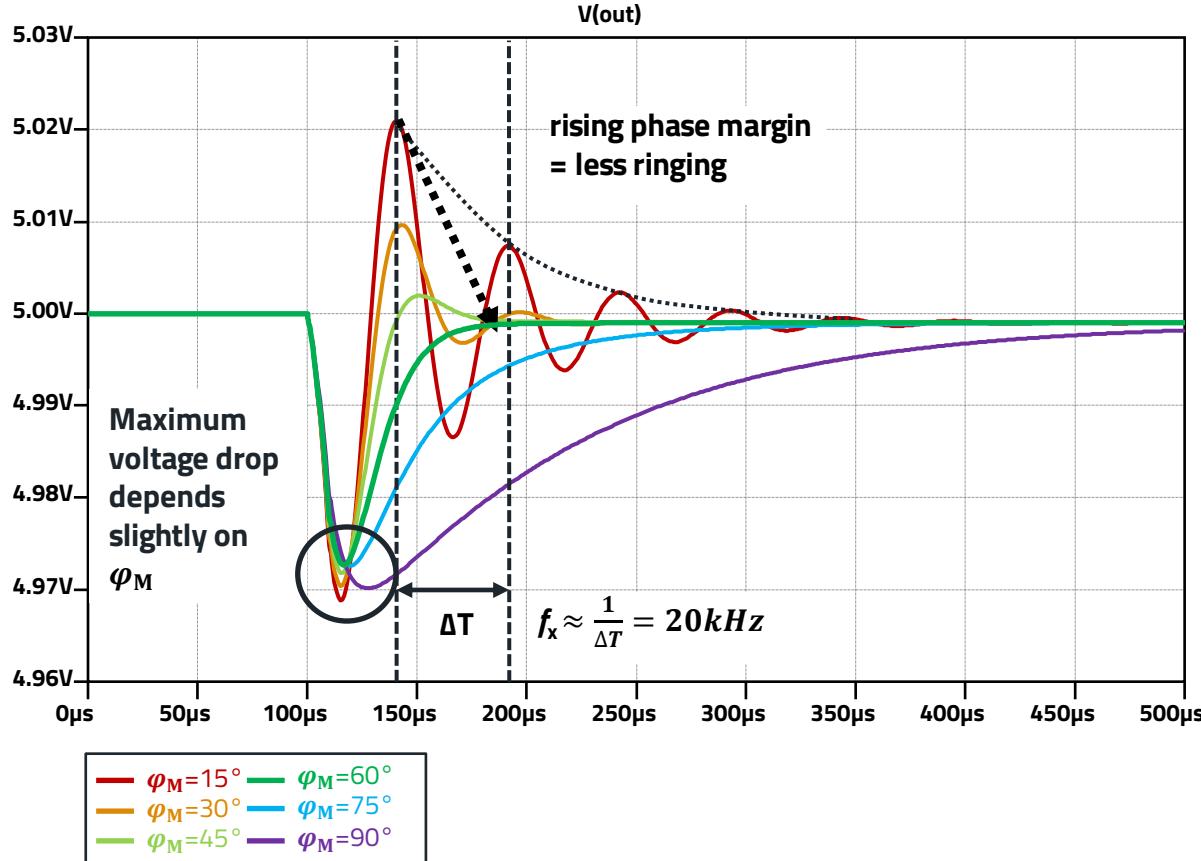Simulation – Buck Demo Board with various compensators



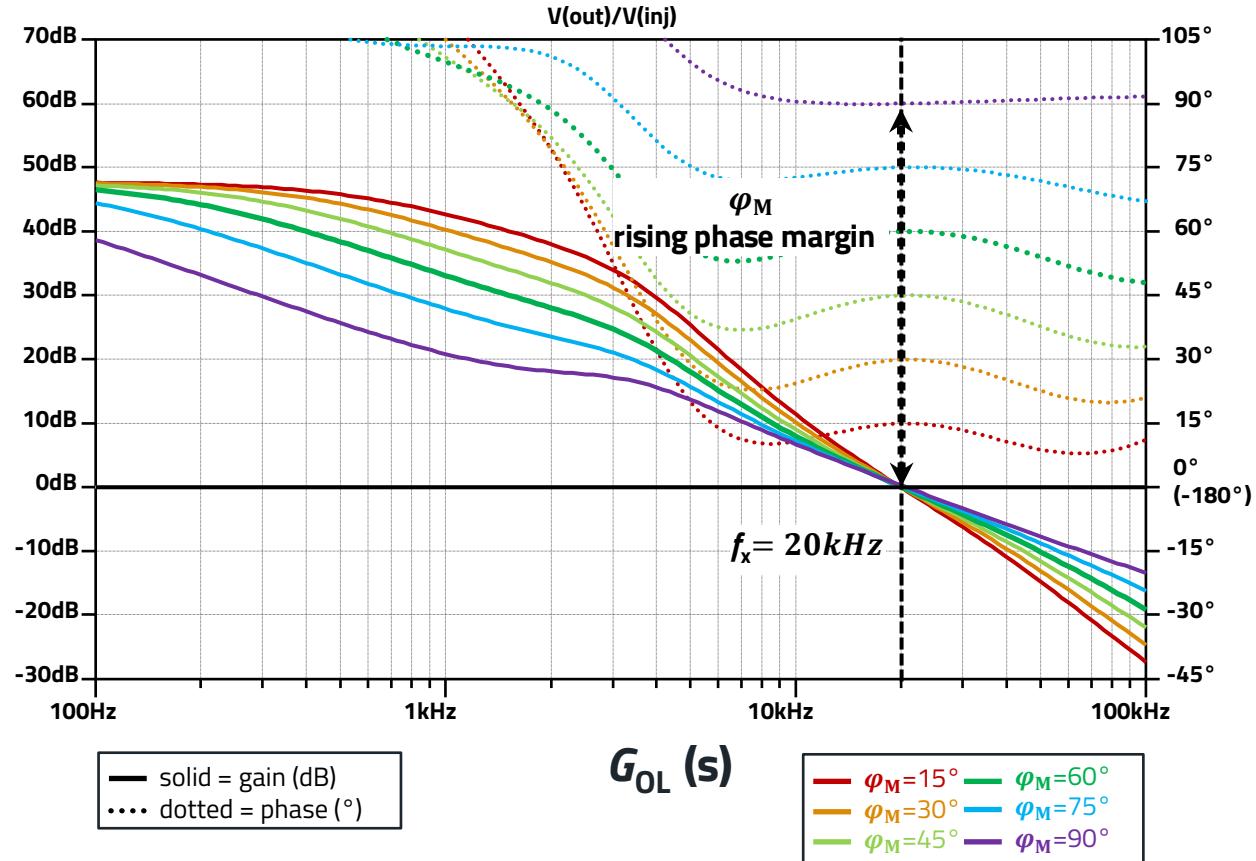
Load step response: $I_{\text{out}} 1\text{A} \rightarrow 2\text{A} / U_{\text{in}}=19\text{V}$




Bode plot - Open loop: $I_{\text{out}}=2\text{A} / U_{\text{in}}=19\text{V}$

IMPACT OF CROSSOVER FREQUENCY

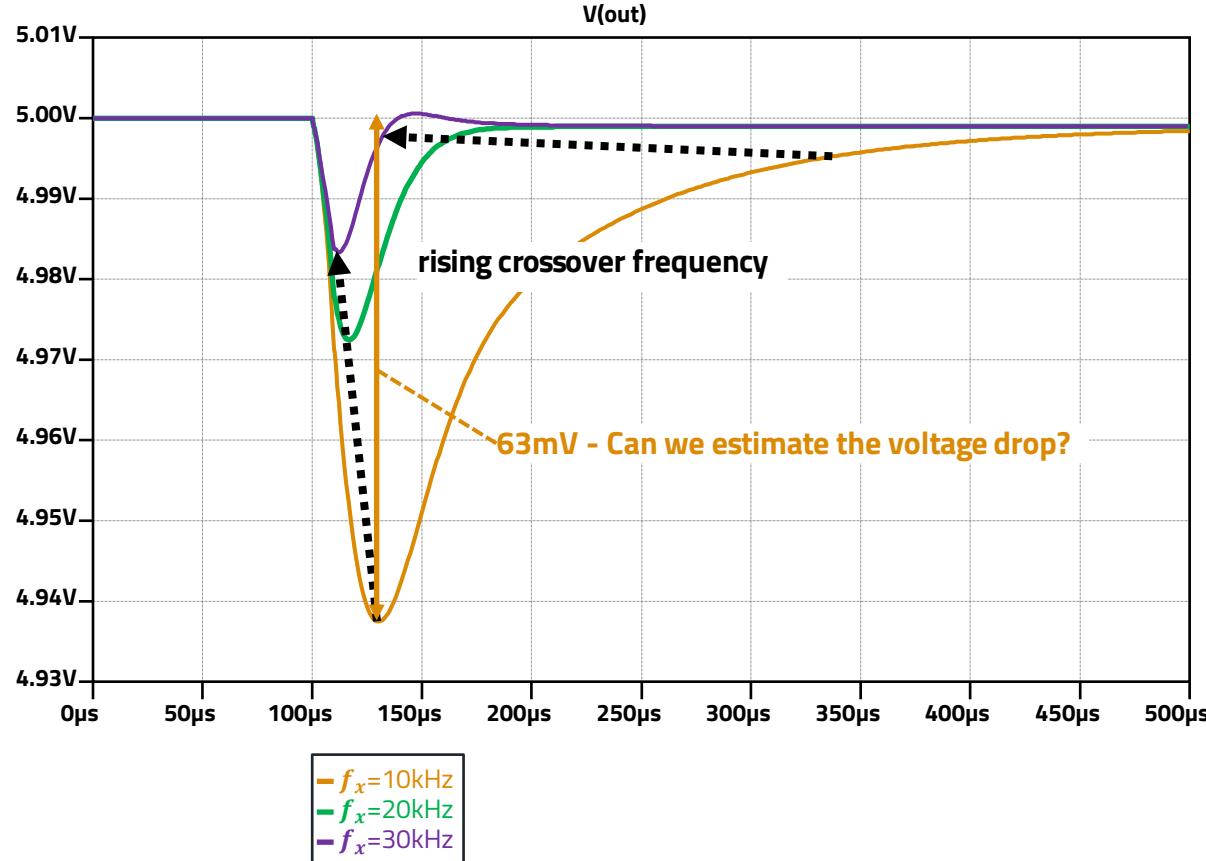Simulation – Buck Demo Board with various compensators



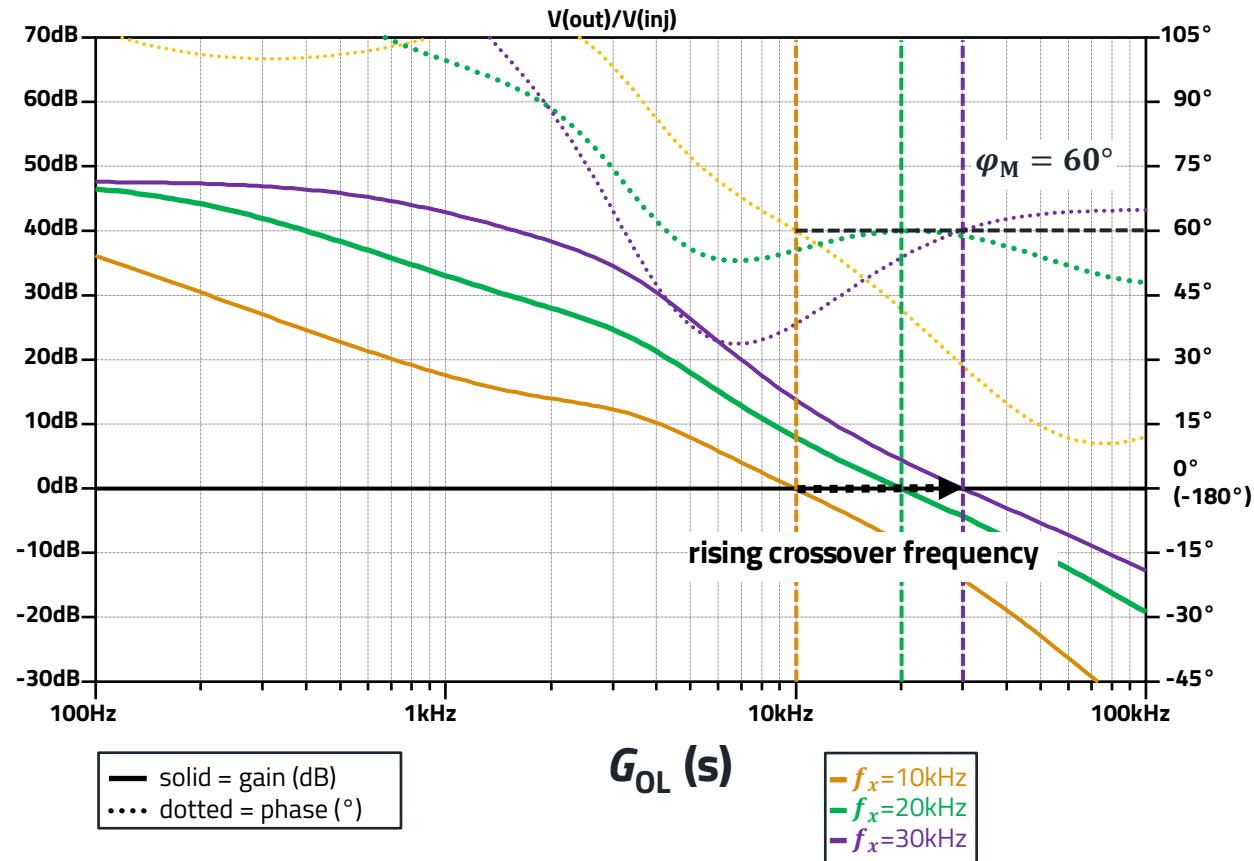Load step response: $I_{\text{out}} 1\text{A} \rightarrow 2\text{A} / U_{\text{in}}=19\text{V}$



Bode plot - Open loop: $I_{\text{out}}=2\text{A} / U_{\text{in}}=19\text{V}$

PLANT TRANSFER FUNCTION

TRANSFER FUNCTION OF THE PLANT

What does it depend on?


- The plant transfer function depends on:
 - Control technique (e.g. voltage- / current-mode control)
 - Topology of the converter (e.g. buck, boost)
 - Conduction mode (DCM – discontinuous conduction mode, CCM – continuous conduction mode)
 - Controller IC (internal gains, compensation ramp)
 - Components used (capacitors, inductors, power semiconductors)
 - Input- and output-voltage
 - Load

TRANSFER FUNCTION OF THE PLANT

Buck Demo Board

General Specification

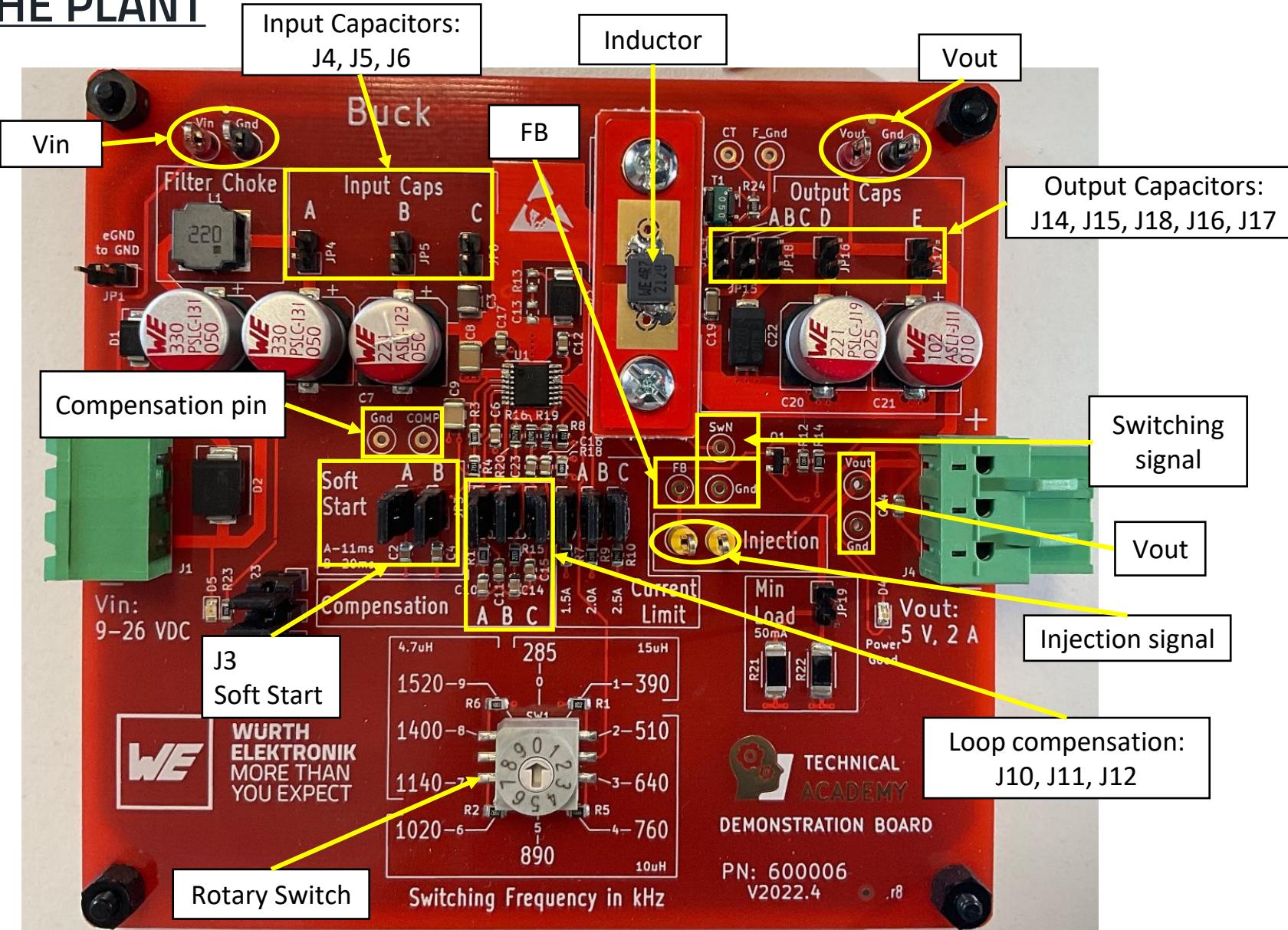
- DC/DC Buck Converter
 - *Voltage Mode control*
 - CCM
 - $V_{in} = 9-26V$
 - $V_{out} = 5V$
 - $I_{out,max} = 2A$
 - $P_{out,max} = 10W$
 - $f_{sw} = 285\text{kHz} - 1.52\text{MHz}$
- Inductor: $10\mu\text{H}/3\text{A}$ WE-LHMI
74437346100
- Control IC: A7987 ST Micro



TRANSFER FUNCTION OF THE PLANT

Schematic and setup - Buck Demo Board

RED EXPERT

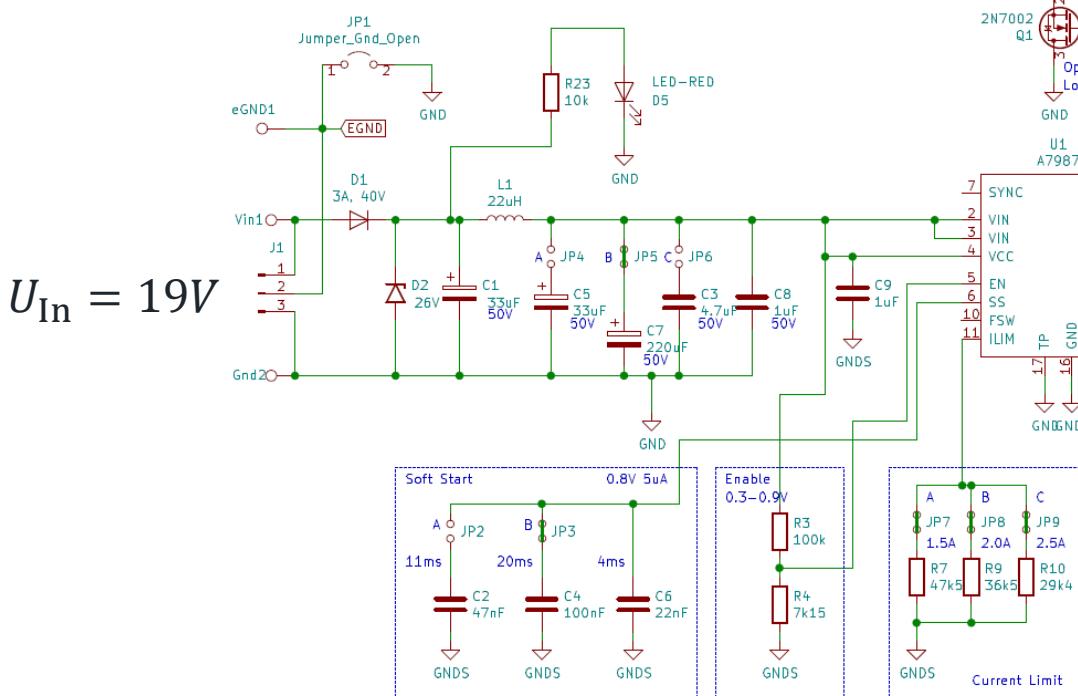

C18

885012207103
WCAP-CSGP
X7R 0805
1μF 50V

C19

885012108021
WCAP-CSGP
X5R 1206
10μF 25V

C22

875015119006
WCAP-PHGP
H-Chip Polymer
220μF 6.3V

ESR @ 20kHz 45mΩ

22mΩ

5mΩ

$$C_{Out_eq} = C18 + C19 + C22 = 227.5\mu F$$

considering DC Bias effect


$$R_{ESR_eq} \approx 20m\Omega$$

at 20kHz & considering jumper resistance, etc.

$$U_{Out} = 5V$$


$$I_{Out} = 2A$$

$$R_{Load} = 2.5\Omega$$

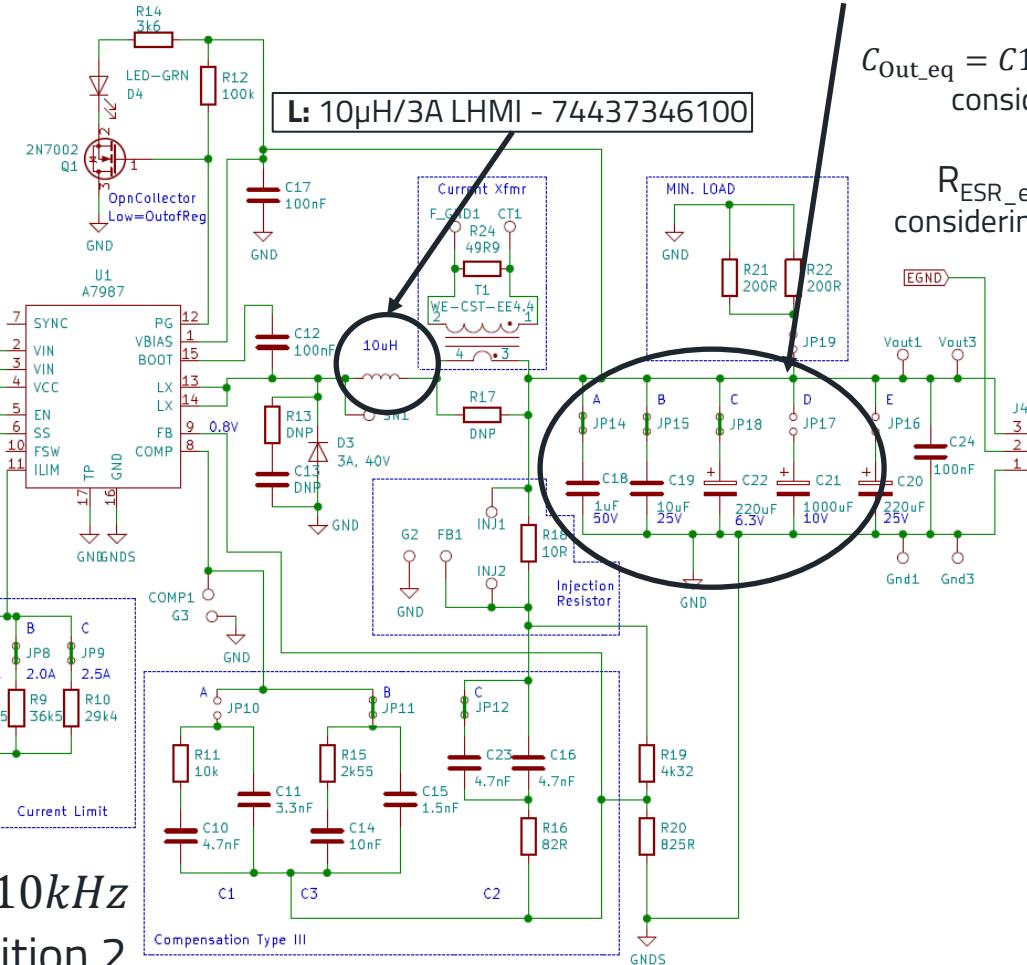

TRANSFER FUNCTION OF THE PLANT

Evaluate the transfer function

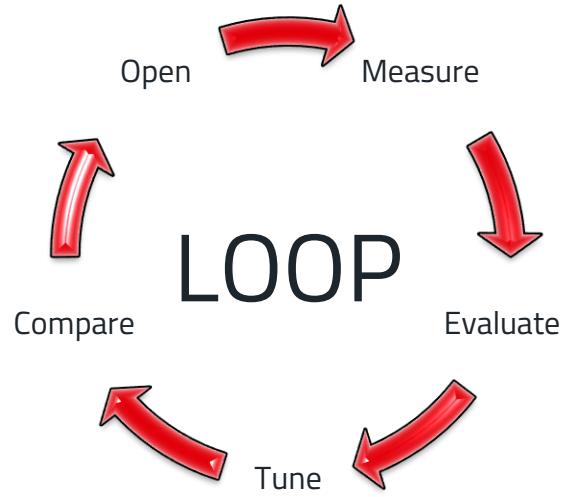

- How?
 - IC **datasheet**
 - **Mathematical** modeling (MATLAB, Mathcad, etc.)
 - **Simulation** (average model of the plant)
 - **Measurements** (used this presentation)

TRANSFER FUNCTION OF THE PLANT

Plant transfer function - model accuracy

$$G_P(s) = A_{\text{PWM}} \cdot \frac{1 + \frac{s}{\omega_{Z,ESR}}}{1 + \frac{s}{Q_0 \cdot \omega_0} + \frac{s^2}{\omega_0^2}}$$

▪ simplified transfer function

- Plant (in CCM) is basically a second-order response (like a LC-filter)
 - LC double pole (complex conjugate pole)
- $\omega_0 = \frac{1}{\sqrt{L \cdot C_{\text{out}}}} \rightarrow f_0 = \frac{1}{2\pi \cdot \sqrt{L \cdot C_{\text{out}}}} \rightarrow f_0 = \frac{1}{2\pi \cdot \sqrt{10\mu H \cdot 227,5\mu F}} \approx 3,338\text{kHz}$

▪ Quality of the LC double pole:

➤ $Q_0 = \frac{R_{\text{Load}}}{\sqrt{C_{\text{out}} \cdot L}} = \frac{2,5\Omega}{\sqrt{227,5\mu F \cdot 10\mu H}} \approx 11.92$

▪ more detailed transfer function


- LC double pole (complex conjugate pole)
- $\omega_0 = \frac{1}{\sqrt{L \cdot C_{\text{out}} \cdot \left(1 + \frac{R_{\text{ESR}}}{R_{\text{Load}}} \right)}} = \frac{1}{\sqrt{10\mu H \cdot 227,5\mu F \cdot \left(1 + \frac{20m\Omega}{2,5\Omega}\right)}} \approx 20,882 \cdot 10^3 \frac{\text{rad}}{\text{s}}$
 $\rightarrow f_0 \approx 3,325\text{kHz}$
- ESR-zero:
- $\omega_{Z,ESR} = \frac{1}{R_{\text{ESR}} \cdot C_{\text{out}}} \rightarrow f_{Z,ESR} = \frac{1}{2\pi \cdot R_{\text{ESR}} \cdot C_{\text{out}}}$
 $\rightarrow f_{Z,ESR} = \frac{1}{2\pi \cdot 20m\Omega \cdot 227,5\mu F} \approx 34,997\text{kHz}$
- Quality of the LC double pole:
- $Q_0 = \frac{1}{\omega_0 \cdot \left(\frac{L}{R_{\text{Load}}} + C_{\text{out}} \cdot \left(R_{\text{ESR}} + \left(1 + \frac{R_{\text{ESR}}}{R_{\text{Load}}} \right) \cdot R_{\text{Ldc}} \right) \right)} = \frac{1}{20,88 \cdot 10^3 \frac{\text{rad}}{\text{s}} \cdot \left(\frac{10\mu H}{2,5\Omega} + 227,5\mu F \cdot \left(20m\Omega + \left(1 + \frac{20m\Omega}{2,5\Omega}\right) \cdot 75m\Omega \right) \right)} \approx 1,86$

As in real life, quality makes the difference!

TRANSFER FUNCTION OF THE PLANT

Bode plot – calculation and measurement (model accuracy)

- The model accuracy depends heavily on the parasitics included
 - Red: Simplified transfer function (Laplace transform) from the slide before
 - Yellow: Transfer function (Laplace transform) including the damping effect and the natural frequency shift of the double pole due the ESR and DCR (inductor)
 - Grey: Measurement of the plant transfer function using RTA4000 Oscilloscope.
- The quality is strongly influenced by the parasitic resistances simulated
- If you start from the simplification, you get an overcompensated control loop
- The ESL has an effect at higher frequencies

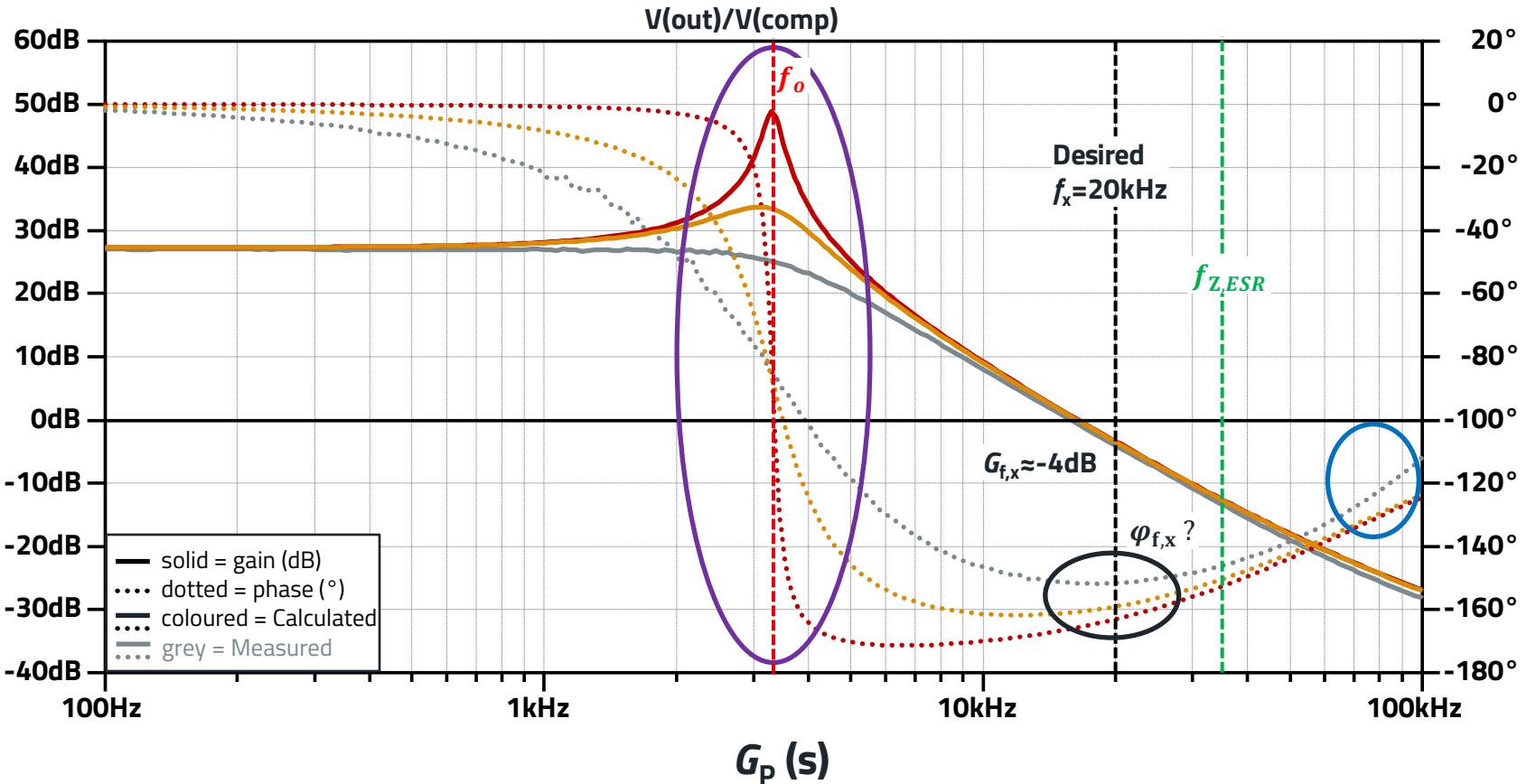


TRANSFER FUNCTION OF THE PLANT

Frequency response measurement - Bode plot

- A small injection resistor is inserted into the feedback voltage divider
 - The injection resistance is small compared to the series resistance of R1 ($4,32\text{k}\Omega$) and R2 (825Ω)
 - The test signal (sinusoidal frequency sweep) is fed in via the injection resistor with an injection transformer

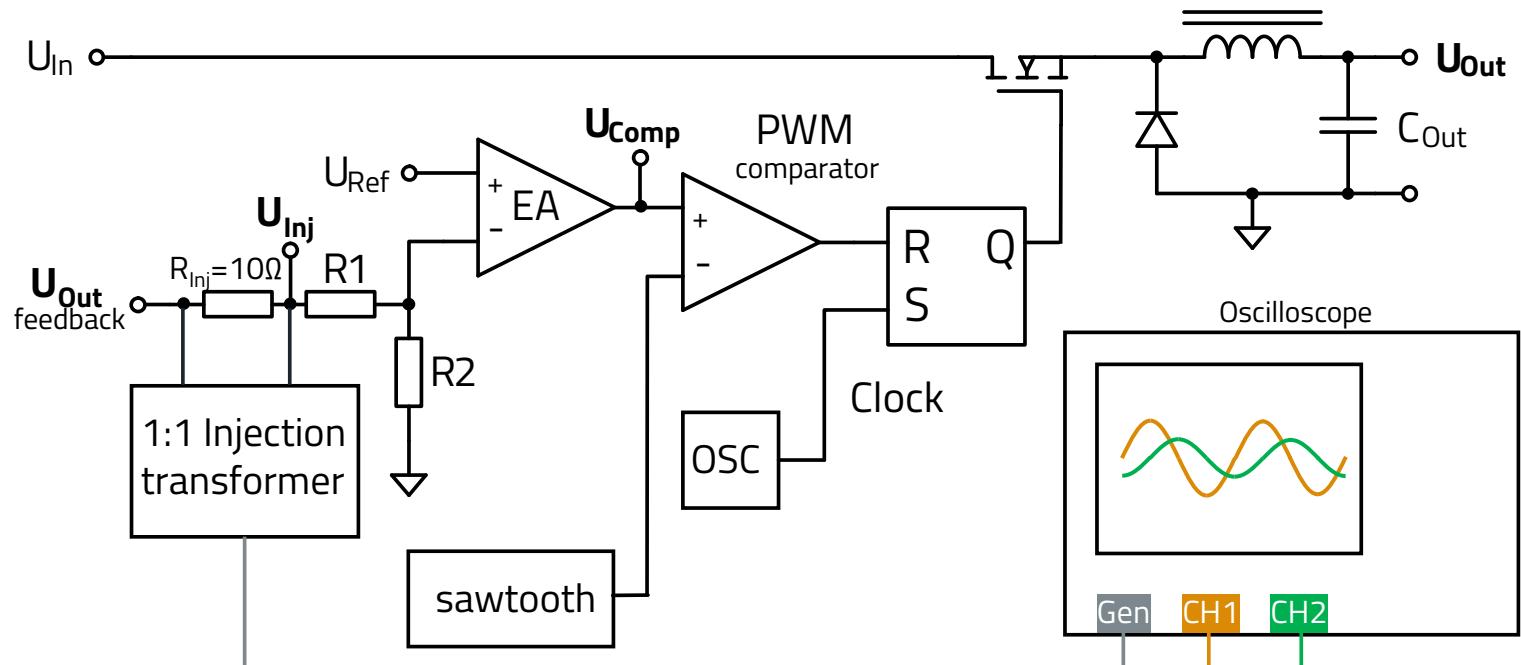
- The oscilloscope plots the gain and the phase by measuring the signal input/output ratio at each test frequency
 - Depending on which input/output ratio is evaluated, the plant, compensator or open loop transfer function can be determined




Transfer function	Input - CH1	Output - CH2
Plant	$G_p(s)$	U_{Comp}
Compensator	$G_c(s)$	U_{Inj}
Open loop	$G_{OL}(s)$	U_{Inj}

TRANSFER FUNCTION OF THE PLANT

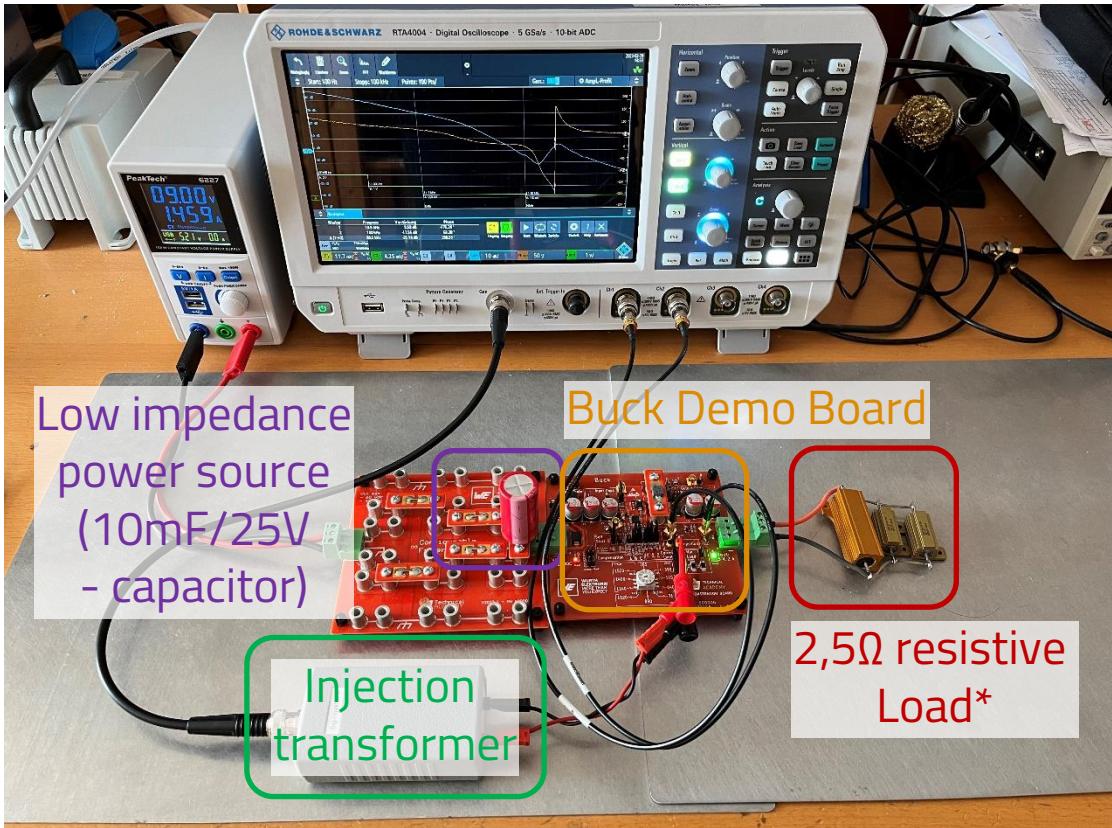Frequency response measurement – Bode plot with RTA4004-K36 (Rohde&Schwarz)



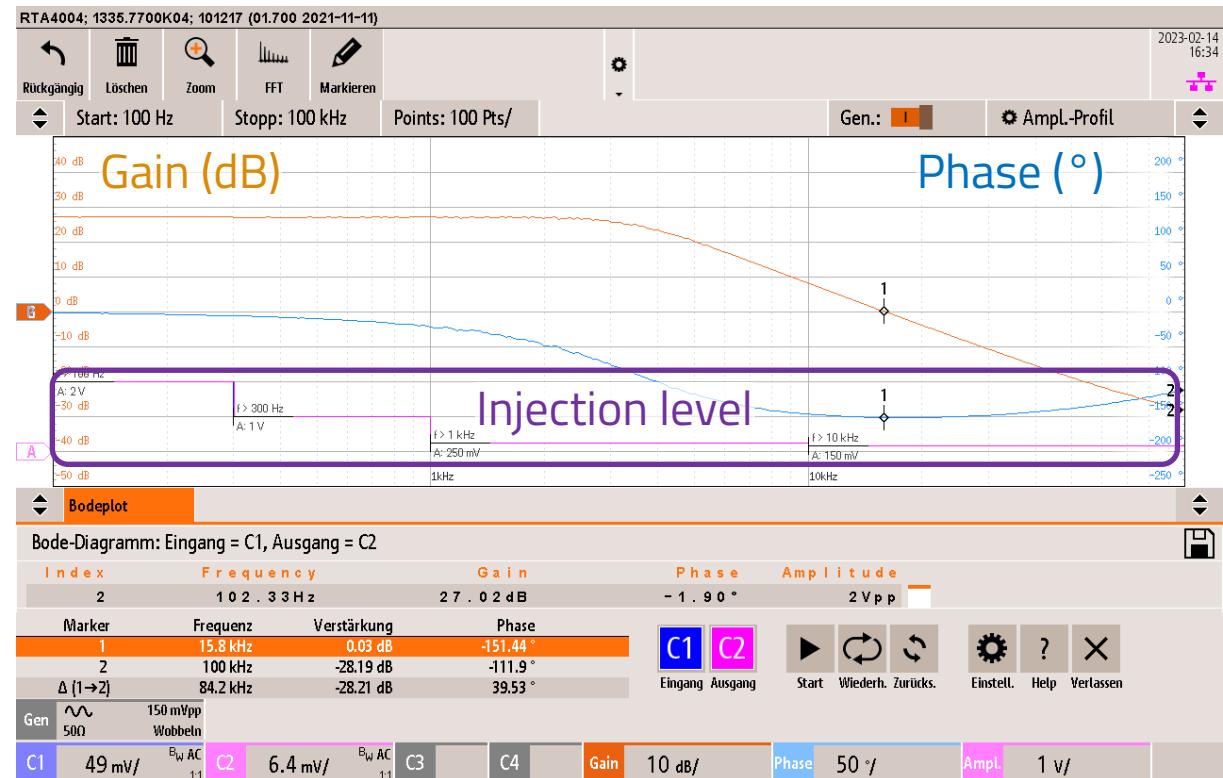*An resistive load is mandatory for frequency response analysis because a controlled electronic load affects the measurement



Measurement

*The injection level must be chosen carefully:
Too big: wrong result (not the small signal behaviour)
Too small: bad SNR (noisy)

COMPENSATOR DESIGN

COMPENSATOR DESIGN

Type III - Compensator


- 1 pole of origin (integrator)
 - High gain at low frequencies
 - Small static error

- 2 poles & 2 zeros

- Gain and phase at crossover frequency can be affected

- Phase boost up to 180°
 - Due 2 zeros
 - Suitable for voltage mode

- Commonly used for voltage mode

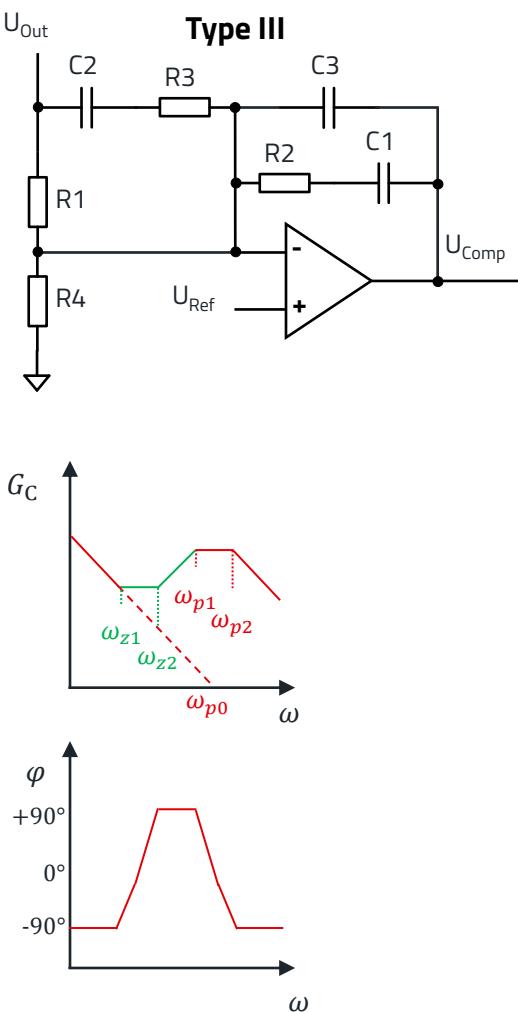

- $$G_C = (-) \frac{\omega_{P0}}{s} \cdot \frac{\left(1 + \frac{s}{\omega_{Z1}}\right) \cdot \left(1 + \frac{s}{\omega_{Z2}}\right)}{\left(1 + \frac{s}{\omega_{P1}}\right) \cdot \left(1 + \frac{s}{\omega_{P2}}\right)}$$


■ Type III:

- $\omega_{Z1} = \frac{1}{R_2 \cdot C_1}$
- $\omega_{Z2} = \frac{1}{C_2 \cdot (R_1 + R_3)}$
- $\omega_{P0} = \frac{1}{R_1 \cdot (C_1 + C_3)}$
- $\omega_{P1} = \frac{(C_1 + C_3)}{R_2 \cdot C_1 \cdot C_3}$
- $\omega_{P2} = \frac{1}{R_3 \cdot C_2}$

COMPENSATOR DESIGN

Type III - Compensator - Design example*

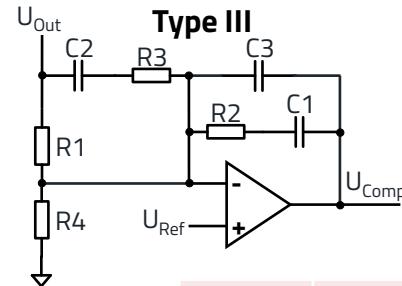*Based on the plant transfer function
of the Buck Demo Board



- Compensator A ($R1=4,33\text{k}\Omega$; $R2=10\text{k}\Omega$; $R3=82\Omega$; $C1=4,7\text{nF}$; $C2=4,7\text{nF}$; $C3=3.3\text{nF}$)
- Compensator B ($R1=4,33\text{k}\Omega$; $R2=2.55\text{k}\Omega$; $R3=82\Omega$; $C1=10\text{nF}$; $C2=4,7\text{nF}$; $C3=1.5\text{nF}$)*
- Compensator B + C ($R1=4,33\text{k}\Omega$; $R2=2.55\text{k}\Omega$; $R3=82\Omega$; $C1=10\text{nF}$; $C2=9,4\text{nF}$; $C3=1.5\text{nF}$)



	Comp A	Comp B	Comp B+C
fz1	3387.99	6244.54	6244.54
fz2	7679.04	7679.04	3839.52
fp0	4596.87	3197.82	3197.82
fp1	8213.32	47874.78	47874.78
fp2	413169.87	413169.87	206584.94

	Comp A	Comp B	Comp B+C
R1	4.33E+03	4.33E+03	4.33E+03
R2	1.00E+04	2.55E+03	2.55E+03
R3	8.20E+01	8.20E+01	8.20E+01
C1	4.70E-09	1.00E-08	1.00E-08
C2	4.70E-09	4.70E-09	9.40E-09
C3	3.30E-09	1.50E-09	1.50E-09

- Different locations for poles and zeros result in different open loop characteristics.
- Optimized performance going from compensator A \rightarrow B \rightarrow B+C.

STABILITY THROUGH THE COMPENSATOR - BUCK DEMO BOARD

Compensator and plant

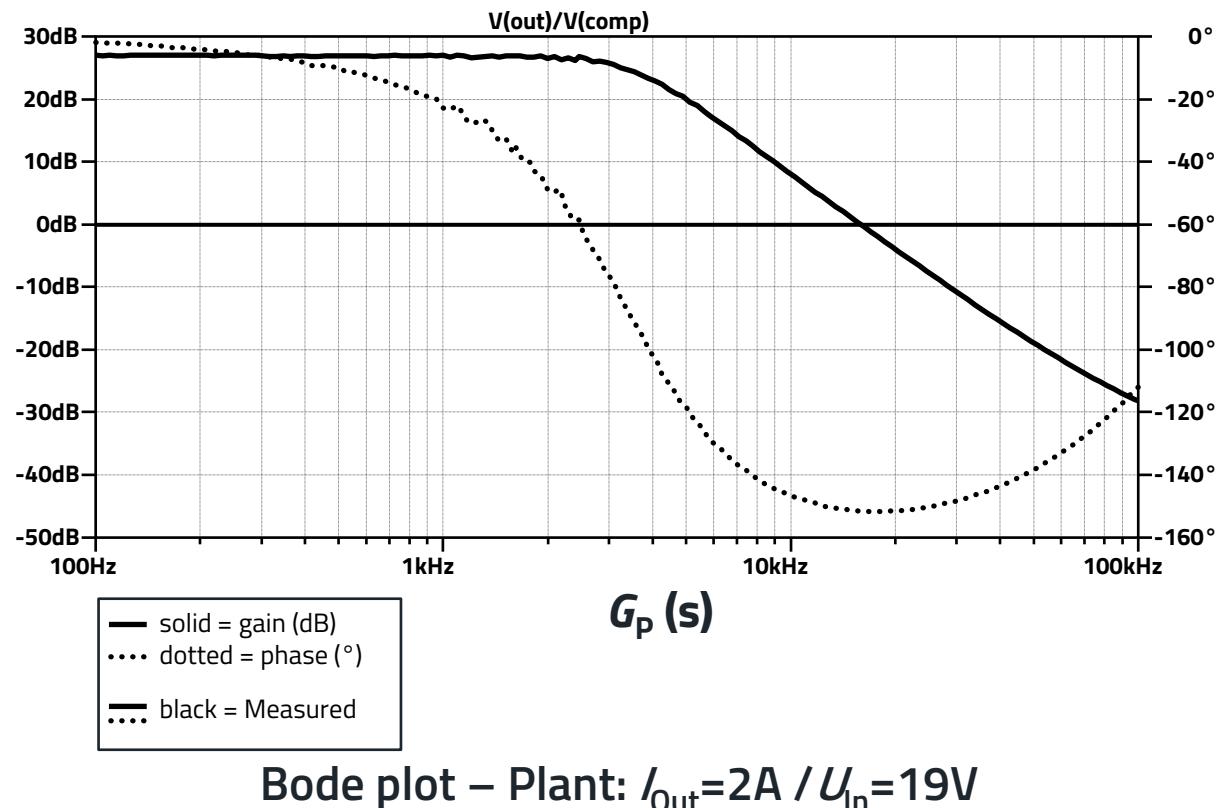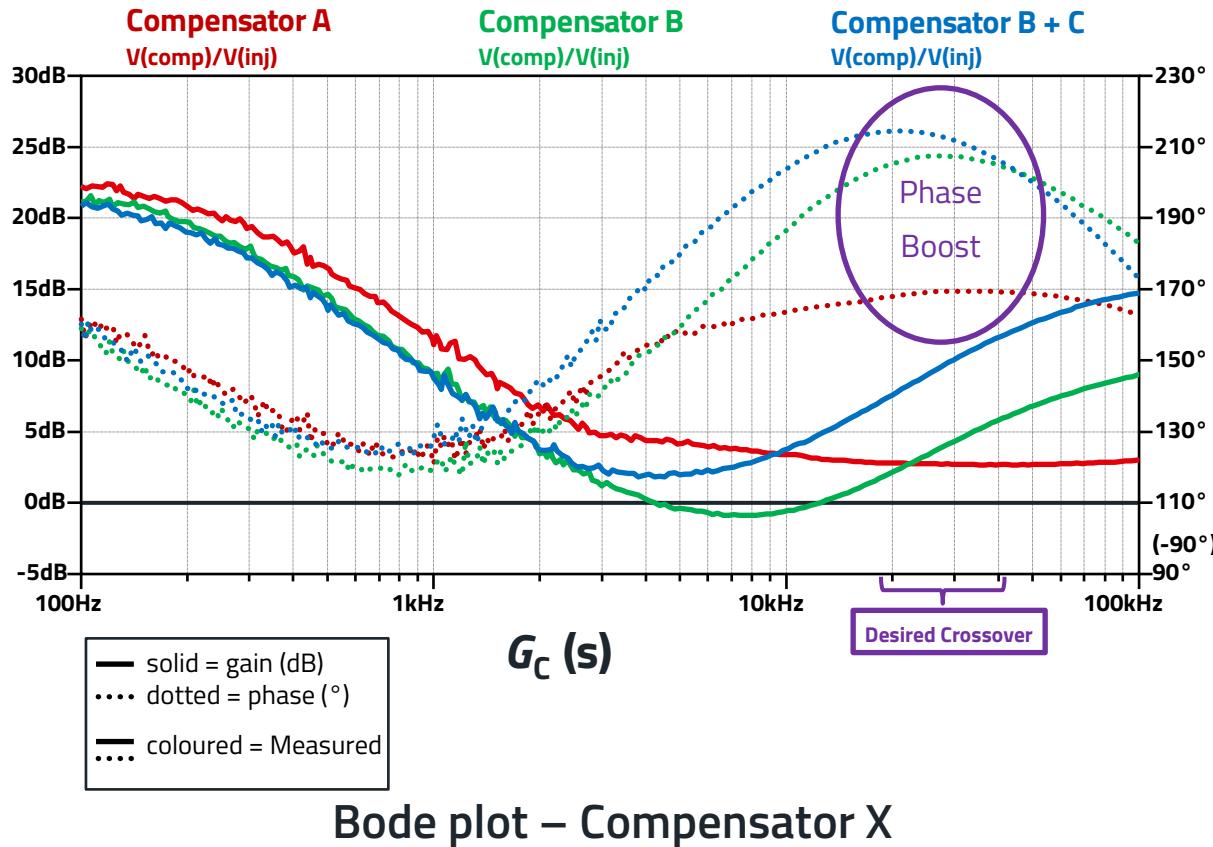

PRACTICAL LOOP MEASUREMENTS

